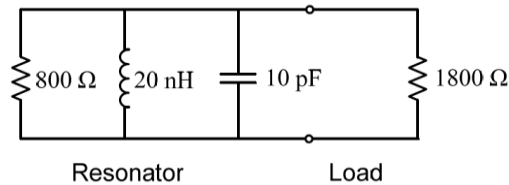


Homework Five


Microwave Resonators, Power Dividers, Couplers, and Filters

Text: Chapter 6-8, 4th Edition, Microwave Engineering, Pozar


1. Consider the loaded parallel resonant RLC circuit shown below. Compute the resonant frequency, unloaded Q , and loaded Q .



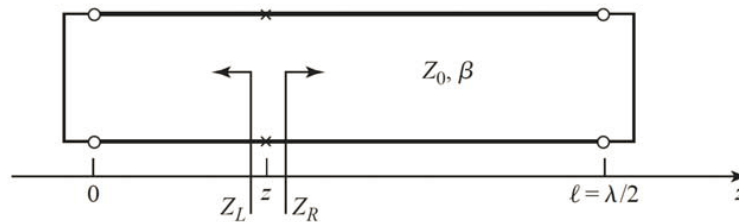2. Consider the resonator shown below, consisting of a $\lambda/2$ length of lossless transmission line shorted at both ends. At an arbitrary point, z , on the line, compute the impedances Z_L and Z_R seen looking to the left and to the right, respectively, and show that $Z_L = Z_R^*$. (This condition holds true for any lossless transmission line resonator and is the basis for the transverse resonance technique discussed in Section 3.9.)




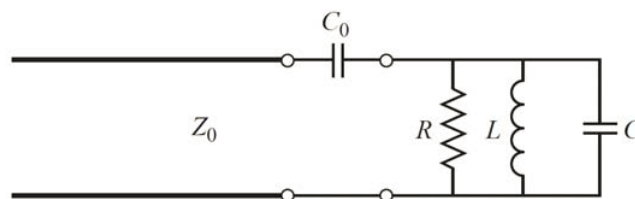3. A parallel RLC circuit, with $R = 1000 \Omega$, $L = 1.26 \text{ nH}$, $C = 0.804 \text{ pF}$, is coupled with a series capacitor, C_0 , to a 50Ω transmission line, as shown below. Determine C_0 for critical coupling to the line. What is the resonant frequency?




4. A 2 W power source is connected to the input of a directional coupler with $C = 20 \text{ dB}$, $D = 25 \text{ dB}$, and an insertion loss of 0.7 dB. Find the output powers (in dBm) at the through, coupled, and isolated ports. Assume all ports to be matched.
5. Design a single-section coupled line coupler with a coupling of 19.1 dB, a system impedance of 60Ω , and a center frequency of 8 GHz. If the coupler is to be made in stripline (edge-coupled), with $\epsilon_r = 2.2$ and $b = 0.32 \text{ cm}$ and $\tan \delta = 0.01$, find the necessary strip widths and separation. Use ADS to plot the S parameters (both amplitude [dB] and phase [deg]) versus frequency in the range of 6-10 GHz.

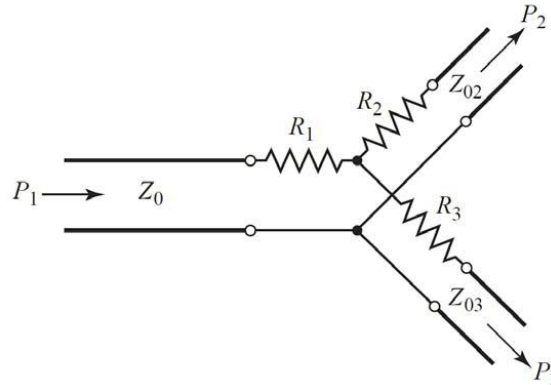
6. Consider the general resistive divider shown below. For an arbitrary power division ratio $\alpha = P_2/P_3$, derive expressions for the resistors R_1 , R_2 , and R_3 , and the output characteristic impedances Z_{o2} and Z_{o3} so that all ports are matched, assuming the source impedance is Z_0 .



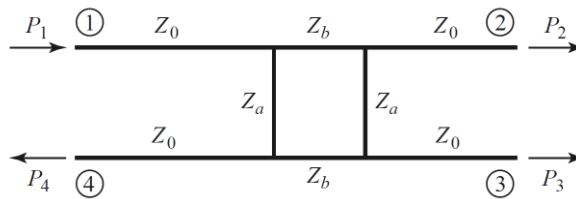
7. Consider the general branch-line coupler shown below, with shunt arm characteristic impedances Z_a and series arm characteristic impedances Z_b . Using an even-odd mode analysis, derive design equations for a quadrature hybrid coupler with an arbitrary power division ratio of $\alpha = P_2/P_3$, and with the input port (port 1) matched. Assume all arms are $\lambda/4$ long. Is port 4 isolated, in general? Validate your design using ADS.



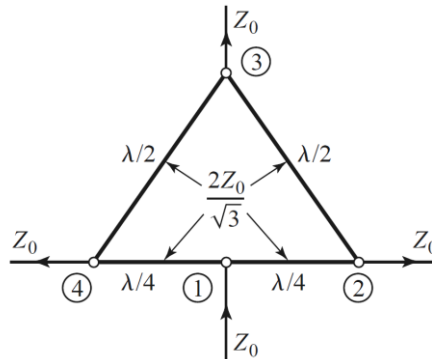8. Find the scattering parameters for the four-port Bagley polygon power divider shown below.



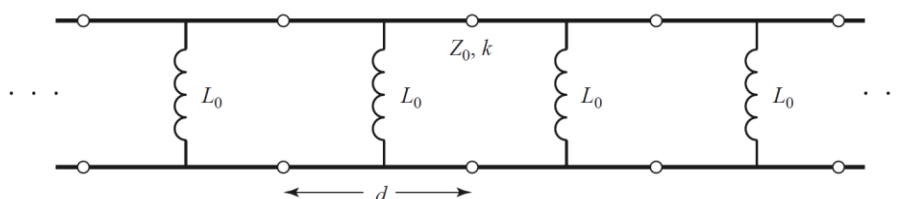9. An input signal V_1 is applied to the sum port of a 180° hybrid, and another signal V_4 is applied to the difference port. What are the output signals?
10. Sketch the k - β diagram for the infinite periodic structure shown below. Assume $Z_0 = 75 \Omega$, $d = 1.0 \text{ cm}$, $k = k_0$, and $L_0 = 1.25 \text{ nH}$.



11. Design a composite low-pass filter by the image parameter method with the following specifications: $R_0 = 50 \Omega$, $f_c = 50$ MHz, and $f_\infty = 52$ MHz. Use ADS to plot the insertion loss versus frequency.
12. Design a low-pass, maximally flat lumped-element filter having a passband of 0–3 GHz, and an attenuation of at least 20 dB at 5 GHz. The characteristic impedance is 75Ω . Use ADS to plot the insertion loss versus frequency.
13. Design a low-pass, fourth-order, maximally flat filter using only shunt stubs. The cutoff frequency is 8 GHz and the impedance is 50Ω . Use ADS to plot the insertion loss versus frequency.
14. Design a stepped-impedance low-pass filter with $f_c = 2.0$ GHz and $R_0 = 50 \Omega$, using the exact transmission line equivalent circuit of Figure 8.39a. Assume a maximally flat $N = 5$ response, and solve for the necessary line lengths and impedances if $Z_l = 10 \Omega$ and $Z_h = 150 \Omega$. Use the software to plot the insertion loss versus frequency.
15. Design a bandpass filter using three quarter-wave short-circuited stub resonators. The filter should have a 0.5 dB equal-ripple response, a center frequency of 3 GHz, a 20% bandwidth, and an impedance of 100Ω . (a) Find the required characteristic impedances of the resonators, and use ADS (**Schematic simulation**) to plot the insertion loss from 1 to 5 GHz. (b) Lay out the microstrip implementation of the filter on a Rogers RO4003 substrate having $\epsilon_r = 3.55$, $d = 0.5$ mm, and $\tan \delta = 0.027$, and with copper conductors $17 \mu\text{m}$ thick (Use **ADS LinCalc** tool to find the microstrip line physical length and width). Use **ADS Momentum** simulation to plot the insertion loss versus frequency in the passband of the filter, and compare with the lossless case.