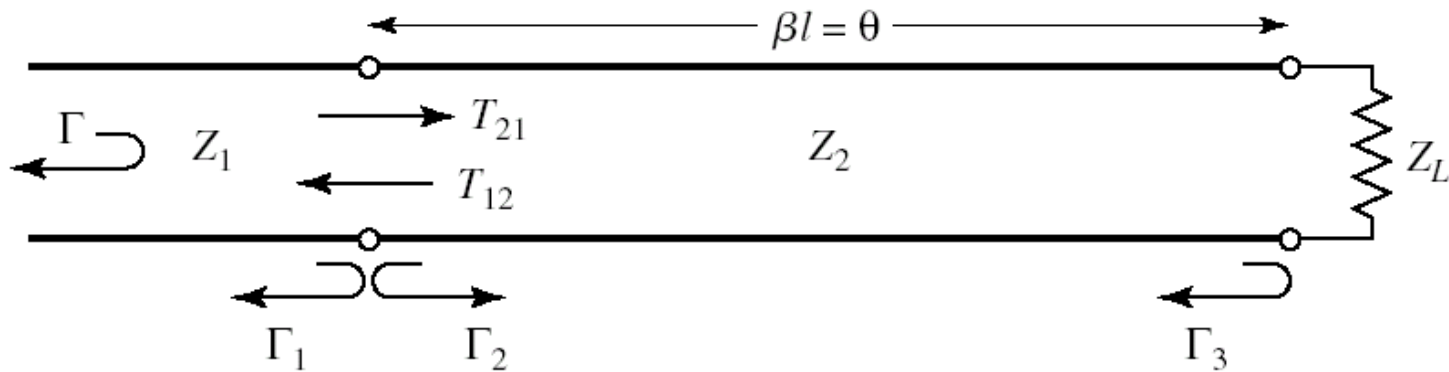


The Theory of Small Reflections

Γ ?




$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

$$\Gamma_2 = -\Gamma_1$$

$$T_{21} = 1 + \Gamma_1 = \frac{2Z_2}{Z_1 + Z_2}$$

$$T_{12} = 1 + \Gamma_2 = \frac{2Z_1}{Z_1 + Z_2}$$
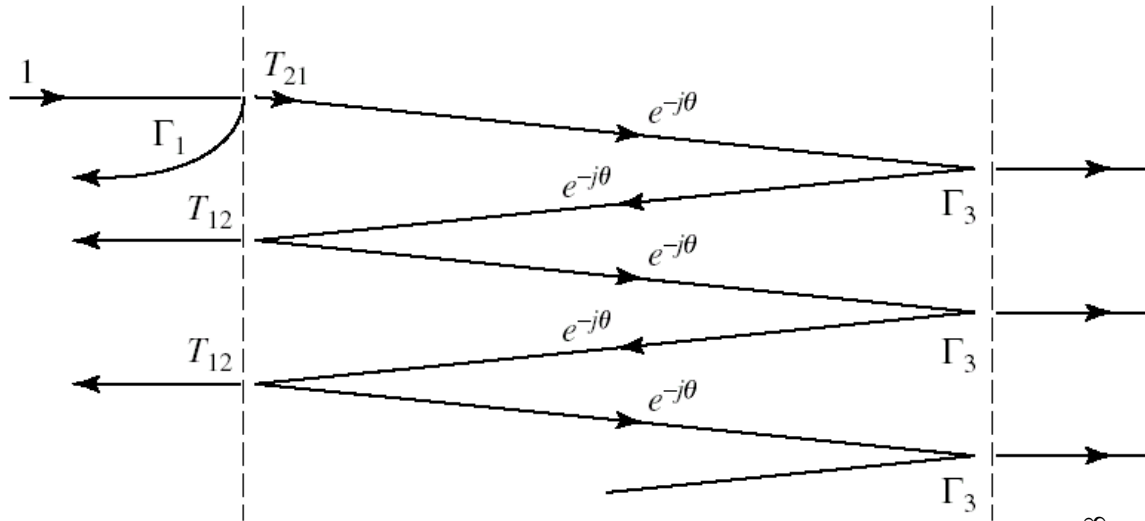
$$\Gamma_3 = \frac{Z_L - Z_2}{Z_L + Z_2}$$



$$\Gamma = \Gamma_1 + T_{12}T_{21}\Gamma_3e^{-2j\theta} + T_{12}T_{21}\Gamma_3^2\Gamma_2e^{-4j\theta} + \dots = \Gamma_1 + T_{12}T_{21}\Gamma_3e^{-2j\theta} \sum_{n=0}^{\infty} \Gamma_2^n \Gamma_3^n e^{-2jn\theta}$$

$$\sum_{n=0}^{\infty} x^n = \frac{1}{1-x} \quad \text{for } |x| < 1$$

$$\Gamma = \Gamma_1 + \frac{T_{12}T_{21}\Gamma_3e^{-2j\theta}}{1 - \Gamma_2\Gamma_3e^{-2j\theta}}$$


$$\begin{aligned} \Gamma_2 &= -\Gamma_1 \\ T_{21} &= 1 + \Gamma_1 = \frac{2Z_2}{Z_1 + Z_2} \\ T_{12} &= 1 + \Gamma_2 = \frac{2Z_1}{Z_1 + Z_2} \end{aligned}$$

$$\Gamma = \Gamma_1 + \frac{(1 + \Gamma_1)(1 - \Gamma_1)\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}} = \Gamma_1 + \frac{(1 - \Gamma_1^2)\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}} = \frac{\cancel{\Gamma_1 + \Gamma_1^2\Gamma_3e^{-2j\theta}} + (1 - \cancel{\Gamma_1^2})\Gamma_3e^{-2j\theta}}{1 + \Gamma_1\Gamma_3e^{-2j\theta}}$$

$$\Gamma = \frac{\Gamma_1 + \Gamma_3 e^{-2j\theta}}{1 + \Gamma_1 \Gamma_3 e^{-2j\theta}}$$

If the discontinuities between the impedances Z_1 , Z_2 , and Z_2 , Z_L are small, then $|\Gamma_1 \Gamma_3| \ll 1$.
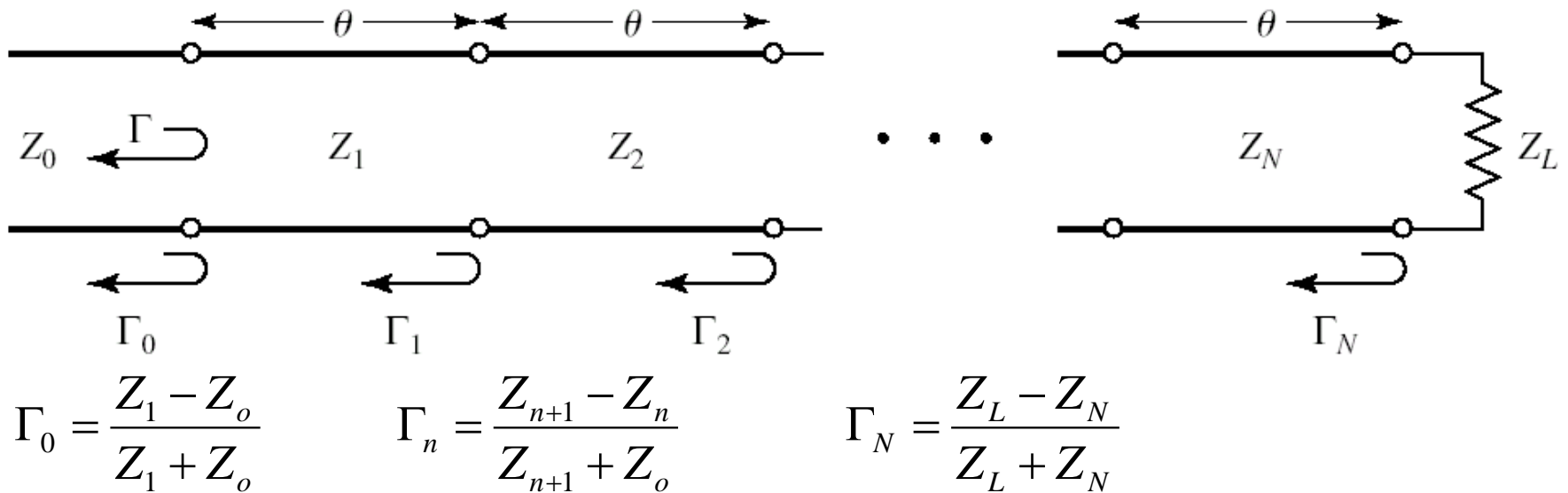
$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-2j\theta}$$



$$\Gamma \cong \Gamma_1 + \Gamma_3 e^{-2j\theta}$$

$$\Gamma = \Gamma(\theta) \cong \Gamma_0 + \Gamma_1 e^{-2j\theta} + \Gamma_2 e^{-4j\theta} + \dots + \Gamma_{N-2} e^{-2j(N-2)\theta} + \Gamma_{N-1} e^{-2j(N-1)\theta} + \Gamma_N e^{-2jN\theta}$$

Assume that the transformer is symmetrical

$$\Gamma_0 = \Gamma_N \quad \Gamma_1 = \Gamma_{N-1} \quad \Gamma_2 = \Gamma_{N-2} \quad \text{etc.}$$

$$\Gamma(\theta) = \Gamma_0 + \Gamma_1 e^{-2j\theta} + \Gamma_2 e^{-4j\theta} + \dots + \Gamma_2 e^{-2j(N-2)\theta} + \Gamma_1 e^{-2j(N-1)\theta} + \Gamma_0 e^{-2jN\theta}$$

$$\Gamma(\theta) = \Gamma_0 (1 + e^{-2jN\theta}) + \Gamma_1 (e^{-2j\theta} + e^{-2j(N-1)\theta}) + \Gamma_2 (e^{-4j\theta} + e^{-2j(N-2)\theta}) + \dots$$

$$\Gamma(\theta) = e^{-jN\theta} \left[\Gamma_0 (e^{jN\theta} + e^{-jN\theta}) + \Gamma_1 (e^{j(N-2)\theta} + e^{-j(N-2)\theta}) + \Gamma_2 (e^{j(N-4)\theta} + e^{-j(N-4)\theta}) + \dots \right]$$

$$\Gamma(\theta) = 2e^{-jN\theta} \left[\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \frac{1}{2} \Gamma_{N/2} \right]$$

For N even

$$\Gamma(\theta) = 2e^{-jN\theta} \left[\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots + \frac{1}{2} \Gamma_{(N-1)/2} \cos \theta \right]$$

For N odd

Finite Fourier Cosine Series

By choosing the Γ_{ns} and enough sections (N) we can achieve the required response.

Binomial Multisection
Matching Transformers

Chebyshev Multisection
Matching Transformers

The Binomial MultiSection Transformer

We first consider the **Binomial Function**:

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N$$


This function has the desirable **properties** that:

$$\begin{aligned}\Gamma(\theta = \pi/2) &= A(1 + e^{-j\pi})^N \\ &= A(1 - 1)^N \\ &= 0\end{aligned}$$

and that:

$$\left. \frac{d^n \Gamma(\theta)}{d\theta^n} \right|_{\theta=\pi/2} = 0 \text{ for } n=1,2,3,\dots,N-1$$

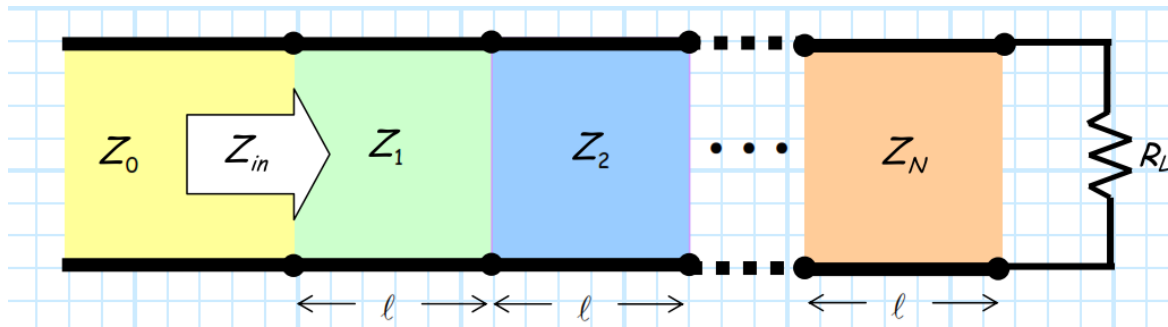In other words, this Binomial Function is **maximally flat** at the Point $\theta=\pi/2$, where it has a value of $\Gamma(\theta=\pi/2) = 0$



Set section lengths ℓ so that they are a **quarter-wavelength** ($\lambda_0/4$) at the design frequency ω_0 .

By letting $f=0$ (or $\theta=0$) the electrical length (βl) of each section will likewise **approach zero**. Thus, the **input impedance** will simply be equal to R_L , thus

$$\Gamma(0) = A 2^N = \frac{R_L - Z_0}{R_L + Z_0} \quad \text{so} \quad A = 2^{-N} \frac{R_L - Z_0}{R_L + Z_0}$$

Let's **expand** of the Binomial Function:

$$\begin{aligned}\Gamma(\theta) &= A(1 + e^{-j2\theta})^N \\ &= A(C_0^N + C_1^N e^{-j2\theta} + C_2^N e^{-j4\theta} + C_3^N e^{-j6\theta} + \dots + C_N^N e^{-j2N\theta})\end{aligned}$$

Where

$$C_n^N = \frac{N!}{(N-n)!n!}$$


Compare this to an **N-section transformer function**:

$$\Gamma_n = A C_n^N$$

Of course, we **also know** that these **marginal reflection** coefficients are physically related to the characteristic impedances of each section as:

$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \quad \longrightarrow \quad Z_{n+1} = Z_n \frac{1 + \Gamma_n}{1 - \Gamma_n} = Z_n \frac{1 + A C_n^N}{1 - A C_n^N}$$

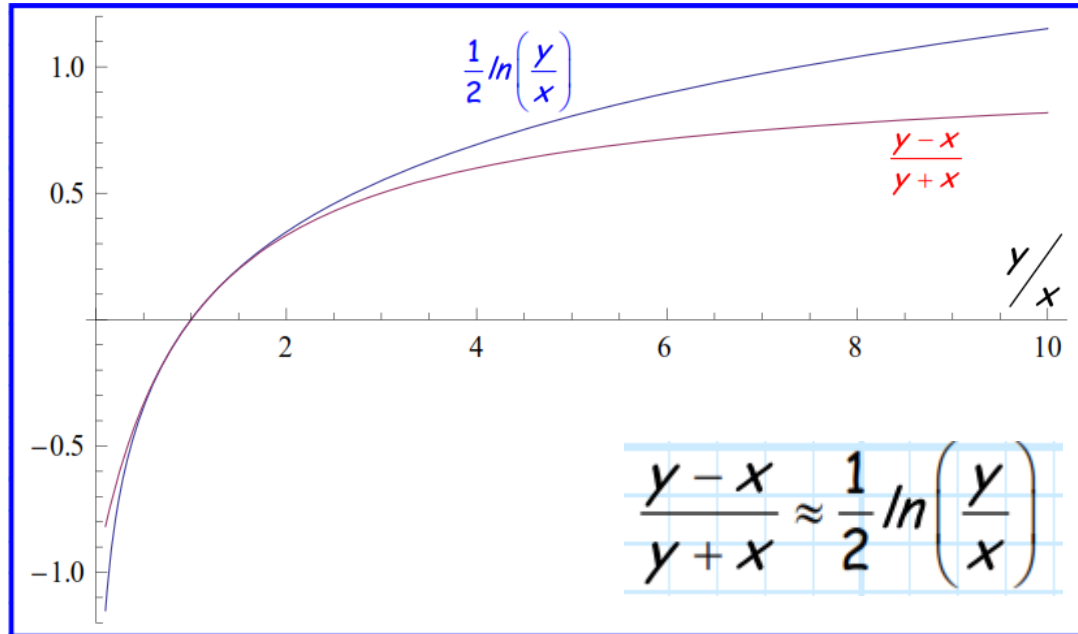You undoubtedly have previously used the approximation:



Now, we know that the values of Z_{n+1} and Z_n in a multi-section matching network are typically **very close**, such that


$$\Gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n} \approx \frac{1}{2} \ln\left(\frac{Z_{n+1}}{Z_n}\right)$$

Then we have


$$Z_{n+1} = Z_n \exp[2\Gamma_n]$$

Where

$$\Gamma_n = A C_n^N$$

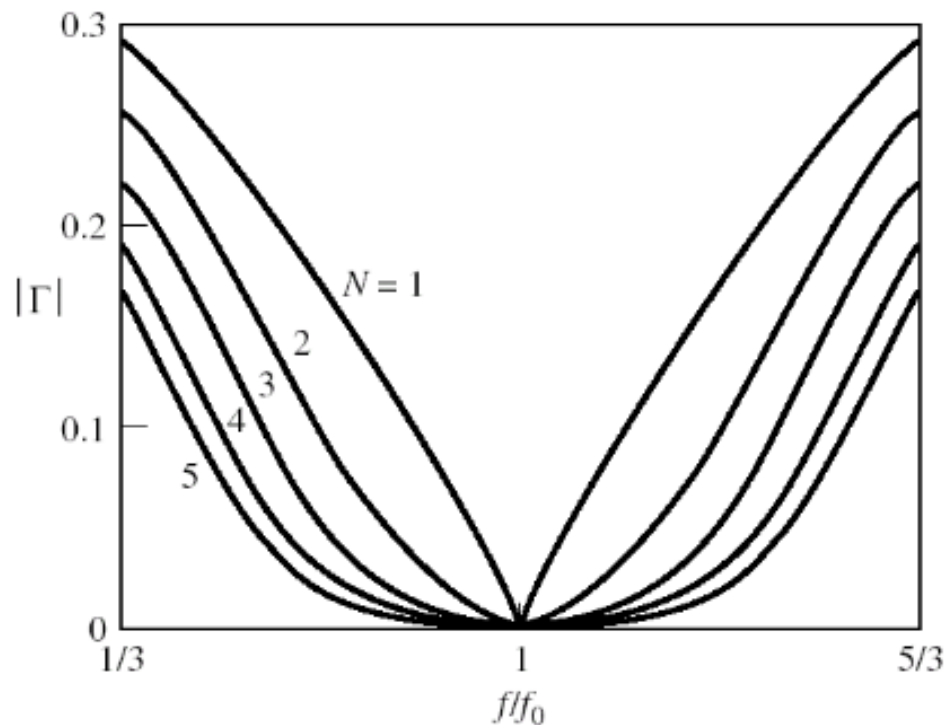

Bandwidth

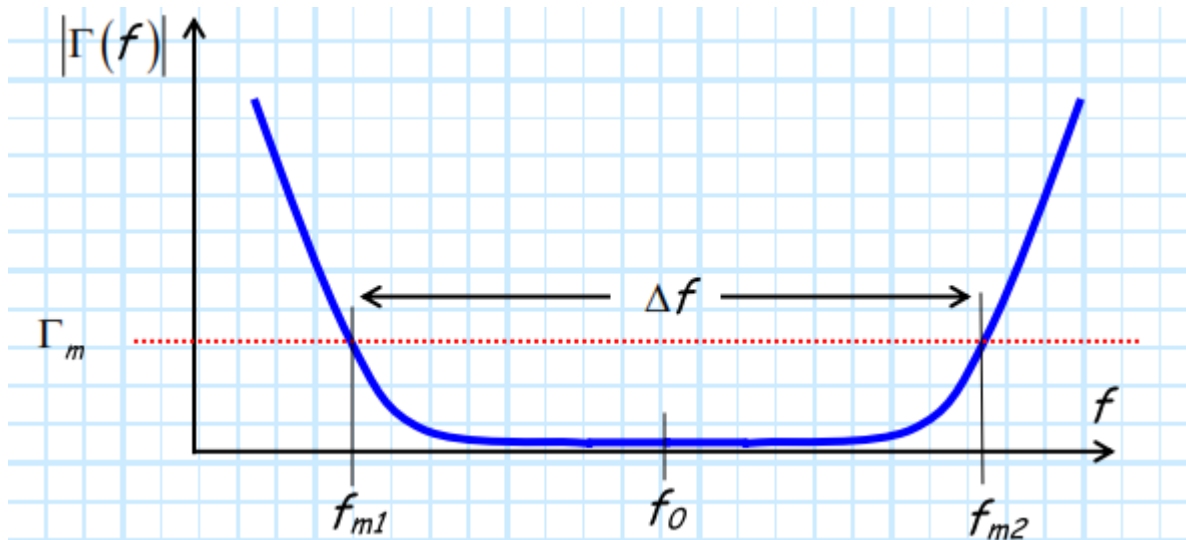

$$\Gamma(\theta) = A(1 + e^{-j2\theta})^N \quad \Rightarrow \quad \begin{aligned} |\Gamma(\theta)| &= 2^N |A| |e^{-jN\theta}| |\cos \theta|^N \\ &= 2^N |A| |\cos \theta|^N \end{aligned}$$

In the figure above Γ_m is maximum allowed reflection

So we have

$$\begin{aligned}\Gamma_m &= |\Gamma(\theta = \theta_m)| \\ &= 2^N |A| |\cos \theta_m|^N\end{aligned}$$


Doing some math we will have

$$\begin{aligned}\theta_{m1} &= \cos^{-1} \left[\frac{1}{2} \left(\frac{\Gamma_m}{|A|} \right)^{1/N} \right] & \theta_{m2} &= \cos^{-1} \left[-\frac{1}{2} \left(\frac{\Gamma_m}{|A|} \right)^{1/N} \right]\end{aligned}$$

On the other word

$$\begin{aligned}\Delta f &= 2(f_0 - f_{m1}) \\ &= 2f_0 - \frac{4f_0}{\pi} \cos^{-1} \left[+\frac{1}{2} \left(\frac{\Gamma_m}{|A|} \right)^{1/N} \right]\end{aligned}$$

Chenushev MultiSection Transformer

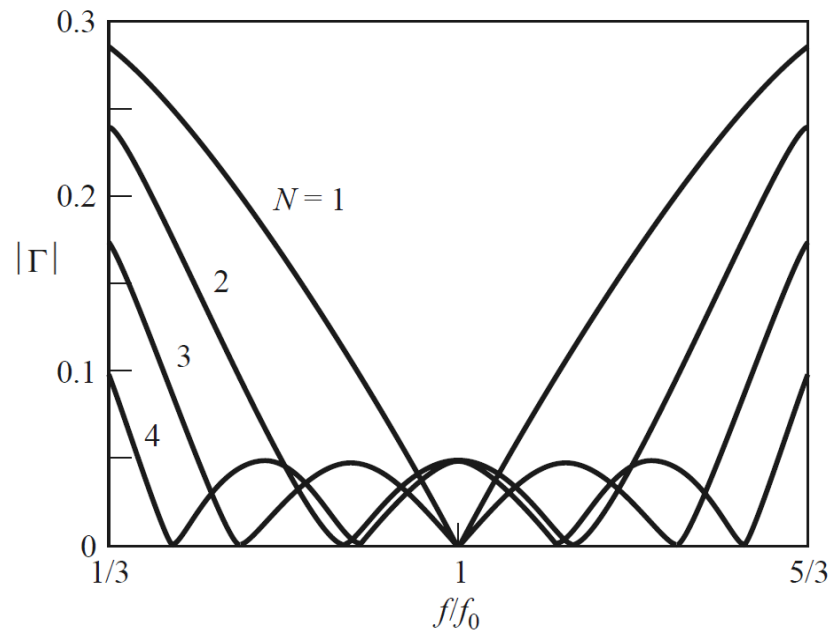

Reading Assignment: section 5.7

Chebyshev Multisection Matching Transformers

- We can also build a multisection matching network such that the function $\Gamma(f)$ is a **Chebyshev function**.
- Chebyshev functions **maximize bandwidth, although at the cost of pass-band ripple**.
- Chebyshev solutions can provide functions $\Gamma(\omega)$ with **wider bandwidth than the Binomial case—although at the “expense” of passband ripple**.
- **Chebyshev transformers are symmetric.**
- The reflection coefficient of a **Chebyshev matching** network has the form:

$$\Gamma(\theta) = A e^{-jN\theta} T_N\left(\frac{\cos \theta}{\cos \theta_m}\right) \quad \text{where } \theta_m = \omega_m T$$
$$= A e^{-jN\theta} T_N(\cos \theta \sec \theta_m)$$

- The function $T_N(\cos \theta \sec \theta)$ is a **Chebyshev polynomial of order N**.


- The first four Chebyshev polynomials are,

$$T_1(x) = x,$$


$$T_2(x) = 2x^2 - 1,$$

$$T_3(x) = 4x^3 - 3x,$$

$$T_4(x) = 8x^4 - 8x^2 + 1.$$

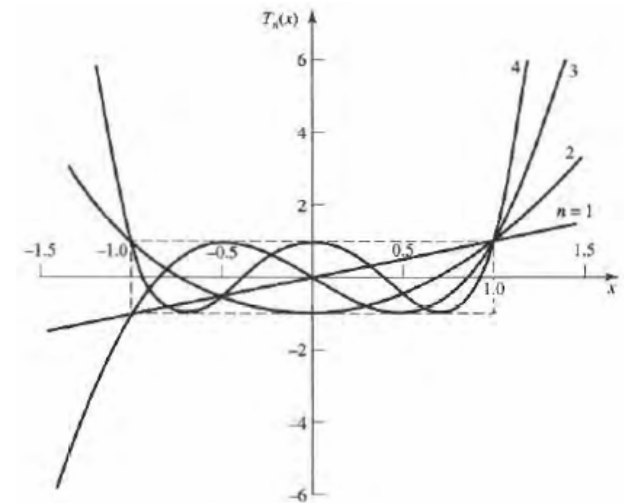

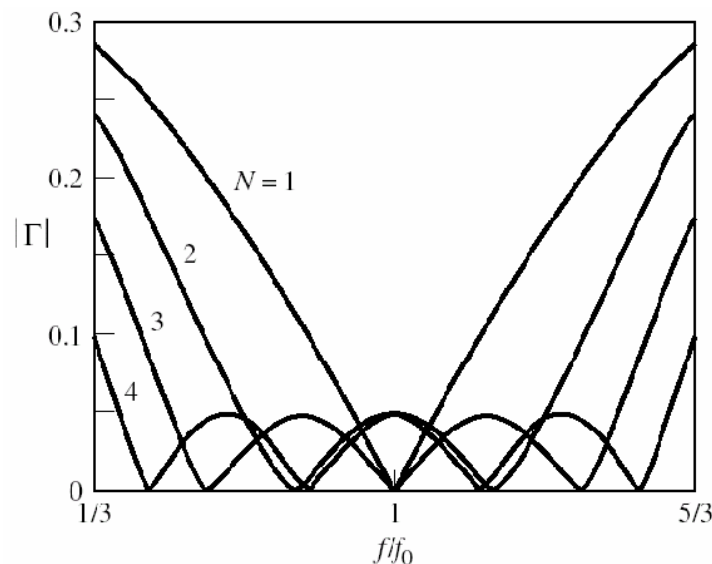- Inserting the **substitution**: $x = \cos\theta \sec\theta_m$ into the Chebyshev polynomials above



$$T_1(\cos\theta \sec\theta_m) = \cos\theta \sec\theta_m$$

$$\begin{aligned} T_2(\cos\theta \sec\theta_m) &= \sec^2\theta_m (1 + \cos 2\theta) - 1 \\ &= \sec^2\theta_m \cos 2\theta + (\sec^2\theta_m - 1) \end{aligned}$$

$$\begin{aligned} T_3(\cos\theta \sec\theta_m) &= \sec^3\theta_m (\cos 3\theta + 3\cos\theta) - 3\sec\theta_m \cos\theta \\ &= \sec^3\theta_m \cos 3\theta + (3\sec^2\theta_m - 3)\sec\theta_m \cos\theta \end{aligned}$$

$$\begin{aligned} T_4(\cos\theta \sec\theta_m) &= \sec^4\theta_m (\cos 4\theta + 4\cos 2\theta + 3) \\ &\quad - 4\sec^2\theta_m (\cos 2\theta + 1) + 1 \\ &= \sec^4\theta_m \cos 4\theta \\ &\quad + 4\sec^2\theta_m (\sec^2\theta_m - 1)\cos 2\theta \\ &\quad + (3\sec^4\theta_m - 4\sec^2\theta_m + 1) \end{aligned}$$

- We can now synthesize a Chebyshev equal-ripple passband by making $\Gamma(\theta)$ proportional to $T_N(\sec\theta_m \cos\theta)$ where N is the number of sections in the transformer.

$$\begin{aligned}\Gamma(\theta) &= 2e^{-jN\theta} [\Gamma_0 \cos N\theta + \Gamma_1 \cos(N-2)\theta + \dots + \Gamma_n \cos(N-2n)\theta + \dots] \\ &= Ae^{-jN\theta} T_N(\sec\theta_m \cos\theta),\end{aligned}$$

- As in the binomial transformer case we can find the constant “A” by letting $\theta = 0$ at zero frequency.


$$\Gamma(0) = \frac{Z_L - Z_0}{Z_L + Z_0} = AT_N(\sec\theta_m), \quad A = \frac{Z_L - Z_0}{Z_L + Z_0} \frac{1}{T_N(\sec\theta_m)}.$$

- The maximum allowable reflection coefficient magnitude in the passband is Γ_m .
- But $\Gamma_m = |A|$
- The maximum value of $T_N(\sec\theta_m \cos\theta)$ is in the passband is unity.
- We can find θ_m by using,

$$\begin{aligned}\sec\theta_m &= \cosh \left[\frac{1}{N} \cosh^{-1} \left(\frac{1}{\Gamma_m} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| \right) \right] \\ &\simeq \cosh \left[\frac{1}{N} \cosh^{-1} \left(\left| \frac{\ln Z_L / Z_0}{2\Gamma_m} \right| \right) \right].\end{aligned}$$

- The fractional bandwidth can be calculated using the following equation once θ_m is known.

$$\frac{\Delta f}{f_0} = 2 - \frac{4\theta_m}{\pi}$$

- Summarizing the Chebyshev matching network design **procedure**
 1. **Determine the value N required to meet the** bandwidth and ripple in Γ requirements.
 2. Determine the **Chebyshev function**. 
 3. Determine all Γ_n by **equating terms with the symmetric multisection transformer** expression:
 4. **Calculate all Z_n using the approximation:**

$$\Gamma_n \simeq \frac{1}{2} \ln \frac{Z_{n+1}}{Z_n}$$

- 5. Determine section **length** $l = \lambda_0/4$.

Tapered Lines

As we know


$$\Delta\Gamma = \frac{(Z + \Delta Z) - Z}{(Z + \Delta Z) + Z} \simeq \frac{\Delta Z}{2Z}.$$

Remember that


$$\frac{d(\ln f(z))}{dz} = \frac{1}{f} \frac{df(z)}{dz}.$$

we will have:
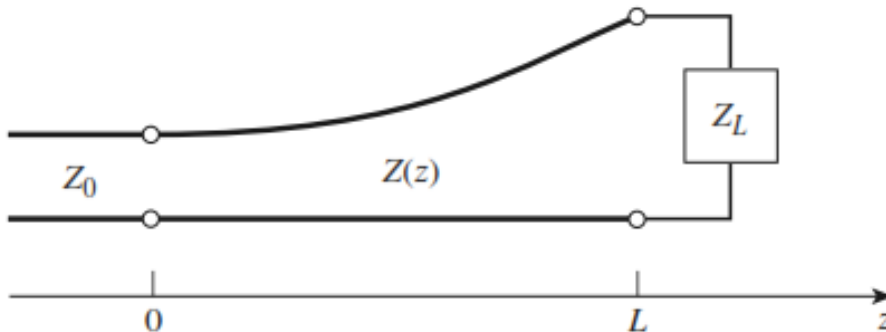
$$d\Gamma = \frac{dZ}{2Z} = \frac{1}{2} \frac{d(\ln Z/Z_0)}{dz} dz,$$



(a)

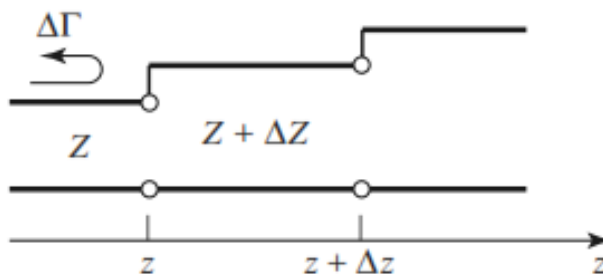

(b)


Finally the reflection coefficient will be

$$\Gamma(\theta) = \frac{1}{2} \int_{z=0}^L e^{-2j\beta z} \frac{d}{dz} \ln \left(\frac{Z}{Z_0} \right) dz,$$


If $Z(z)$ is known, $\Gamma(\theta)$ can be found as a function of frequency. Alternatively, if $\Gamma(\theta)$ is specified, then in principle $Z(z)$ can be found by inversion. This latter procedure is difficult, and is generally avoided in practice

Exponential Taper
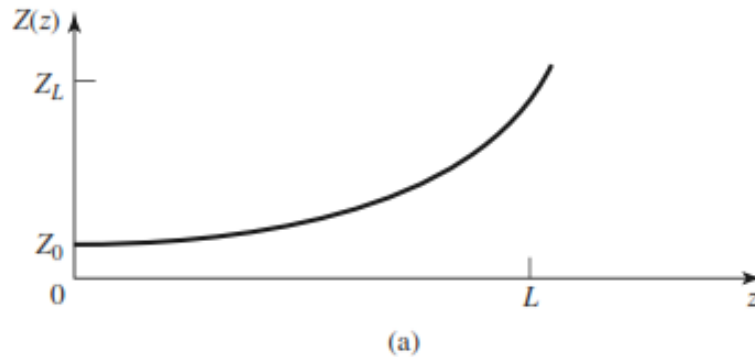
$$Z(z) = Z_0 e^{az} \quad \text{for } 0 < z < L,$$




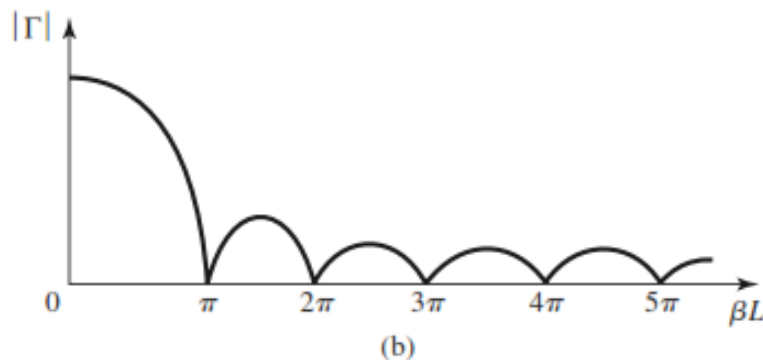
$$a = \frac{1}{L} \ln \left(\frac{Z_L}{Z_0} \right).$$



$$\begin{aligned} \Gamma &= \frac{1}{2} \int_0^L e^{-2j\beta z} \frac{d}{dz} (\ln e^{az}) dz \\ &= \frac{\ln Z_L / Z_0}{2L} \int_0^L e^{-2j\beta z} dz \\ &= \frac{\ln Z_L / Z_0}{2} e^{-j\beta L} \frac{\sin \beta L}{\beta L}. \end{aligned}$$

Triangular Taper
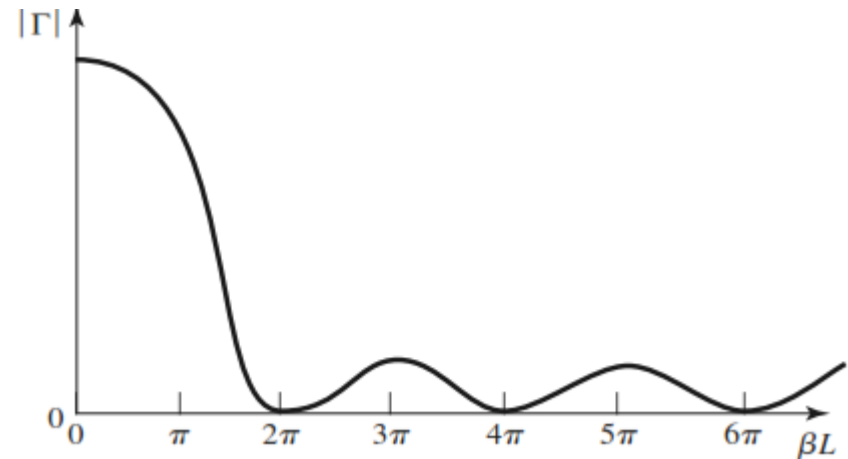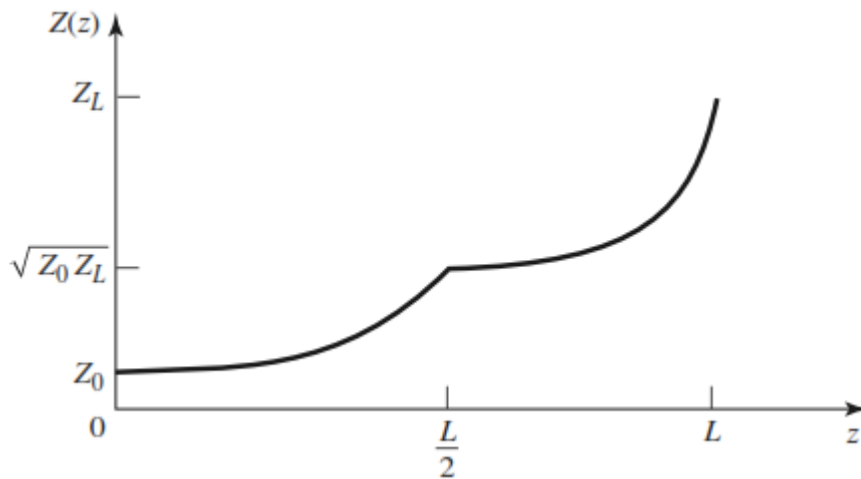
$$Z(z) = \begin{cases} Z_0 e^{2(z/L)^2 \ln Z_L/Z_0} & \text{for } 0 \leq z \leq L/2 \\ Z_0 e^{(4z/L - 2z^2/L^2 - 1) \ln Z_L/Z_0} & \text{for } L/2 \leq z \leq L, \end{cases}$$



$$\Gamma(\theta) = \frac{1}{2} e^{-j\beta L} \ln \left(\frac{Z_L}{Z_0} \right) \left[\frac{\sin(\beta L/2)}{\beta L/2} \right]^2.$$

Klopfenstein Taper

$$\ln Z(z) = \frac{1}{2} \ln Z_0 Z_L + \frac{\Gamma_0}{\cosh A} A^2 \phi(2z/L - 1, A) \quad \text{for } 0 \leq z \leq L,$$

where

$$\phi(x, A) = -\phi(-x, A) = \int_0^x \frac{I_1(A\sqrt{1-y^2})}{A\sqrt{1-y^2}} dy \quad \text{for } |x| \leq 1,$$

And I_1 is modified Bessel function

It can be shown that

$$\Gamma(\theta) = \Gamma_0 e^{-j\beta L} \frac{\cos \sqrt{(\beta L)^2 - A^2}}{\cosh A} \quad \text{for } \beta L > A.$$

where

$$\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} \simeq \frac{1}{2} \ln \left(\frac{Z_L}{Z_0} \right)$$

Clearly

$$\Gamma_m = \frac{\Gamma_0}{\cosh A}$$

