

Power Dividers and Directional Couplers

- Passive components used for power division or power combining
- In the form of three-port (T-junction) networks and fourport (directional) networks



Basic Properties of Dividers and Couplers

Three-Port Networks (T-Junctions)

It would be useful to have a passive lossless network that divides input port power at any port between the other two ports while being matched at all three ports. This would require the network to be <u>matched</u>, <u>lossless</u> and <u>reciprocal</u>.





Therefore, using "normal" lossless components such as transmission lines, capacitors and inductors it is impossible to construct a 3-port network matched at all 3 ports.

Need to relax one of the restrictions.

A. For a <u>nonreciprocal 3-port network</u> $(S_{ij} \neq S_{ji})$, using anisotropic materials (such as ferrite), all ports can be matched and a <u>circulator</u> is created.







Applications of Circulators:

- Protects a power amplifier from output mismatch.
- Allows a transmitter and receiver to share an antenna.





C. For a <u>reciprocal and all-matched 3-port network</u> $(S_{ij} = S_{ji})$, but with lossy components.

This is the case of the resistive divider. A lossy 3-port network can be made to have isolation between its output ports.

Four Port Networks (Directional Couplers)

Pozar shows that a matched, reciprocal, lossless four-port network is possible, and that it has directional coupling between pairs of ports.

There are two possible forms of [S] for a directional coupler, one with outputs differing by 90° in phase and the other with outputs differing by 180° in phase. Any 90° coupler can be made into a 180° coupler by adding a 90° transmission to one port, and *vice versa*.



Dr. Vahid Nayyeri



Any 90° coupler can be made into a 180° coupler by adding a 90° transmission to one port, and *vice versa*. The 90° coupler is referred to as a quadrature hybrid, and can be created using directly connected branch lines between two transmission lines or by means of coupled transmission lines.



Dr. Vahid Nayyeri



Coupling, Directionality and Isolation

Coupling = $C = 10\log(P1/P3) = -20\log\beta dB$

Directivity = D = 10 log (P3/P4) = $20\log\beta/|S_{14}|$ dB

Isolation = I = $10\log(P1/P4) = -20\log|S_{14}| dB$

I = D + C dB



Dr. Vahid Nayyeri

The (3-port) T-Junction Power Divider

Lossless 3-port netowork





If we relax the requirement for matched ports, we can realize tee networks that divide power and provide a match at one port (typically chosen as the input port).

$$Y_{in} = jB + \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_0}$$

For a lossless network, all the characteristic impedances are real, and we can assume B = 0. Then $\underline{Y_o} = \underline{Y_1} + \underline{Y_2}$.

The voltage V_0 at the junction is the same for line 1 and line 2, and the power in the lines is

$$\frac{P_1 = V_0^2 Y_1/2}{\text{so the power division ratio r is}} \quad r = \frac{P_2}{P_1} = \frac{Y_2}{Y_1} = \frac{Z_1}{Z_2}$$



Dr. Vahid Nayyeri

Substituting
$$Y_2 = rY_1$$
 we have $Y_0 = Y_1(1+r)$, so $Z_1 = Z_0(1+r)$
and $Z_2 = Z_0 \frac{1+r}{r}$

The output line impedances Z_1 and Z_2 can be selected to provide various power division ratio. If we let r = 1, we get *even power division* (power split, -3 dB), and $Z_1 = 2 Z_0$, $Z_2 = 2 Z_0$. If needed, the quarter-wave transformers can be used to bring the output line impedances back to the desired level.

If *B* is not negligible, some type of tuning element can usually be added to the divider to cancel this susceptance.

Output ports are not isolated.

Example 7.1 of Pozar!



Resistive Divider





The input impedance of the divider is

$$Z_{in} = \frac{Z_0}{3} + \frac{2Z_0}{3} = Z_0 \quad \longrightarrow \text{ matched}$$

Since the network is symmetric from all three ports, the output ports are also matched.

Output Power

The output voltage from port 2 and 3 are, $V_2 = V_3 = \frac{V_1}{2}$

Thus, $S_{21} = S_{31} = S_{23} = 1/2$, which indicates 6 dB below the input power level. We have

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix} \xrightarrow{\text{Port 2 and 3 are}} P_2 = P_3 = \frac{1}{4} P_{in}$$



The Wilkinson Power Divider

Motivation: to solve the problem of output isolation

The Wilkinson power divider is a three-port that has all ports matched with isolation between the two output ports.



The Wilkinson power divider can be made to give arbitrary power division. But an equal-split one is used here for analysis.



Features of the Wilkinson dividers

1. By choosing the impedance of the $\lambda/4$ lines to be $\sqrt{2} Z_o$, the matched output loads $Z_L = Z_o$ are transformed to $2Z_o$ so they can be placed in parallel to equal $2Z_o/2 = Z_o$ creating a matched condition at the input port.

2. Any mismatched power returned from a load at either output port is divided equally between the load on the input port (the generator source impedance, presumed to be $Z_g = Z_o$) and the resistor R.

3. None of the reflected power from a mismatched load is dissipated in the other load, so the output ports are isolated ($S_{23} = S_{32} = 0$).



Even-Odd Mode Analysis





Even mode:
$$V_{g2} = V_{g3} = 2V$$

No current (o.c.) flows through the resistors between port 2 and 3 or the short circuit at port 1.





Setting up x coordinate as shown in the figure. Looking toward the left from port 1, the transmission line voltage can be written as

$$V(x) = V^+ (e^{-j\beta x} + \Gamma e^{j\beta x})$$

Then,

$$V_2^e = V(-\lambda/4) = jV^+(1-\Gamma) = V$$

$$V_1^e = V(0) = V^+(1+\Gamma) = jV\frac{\Gamma+1}{\Gamma-1}$$
We have

$$\Gamma = \frac{2-\sqrt{2}}{2+\sqrt{2}}$$
therefore, $V_1^e = -jV\sqrt{2}$



Odd mode: $V_{g2} = -V_{g3} = 2V$

From symmetry point of view, the middle point of the equivalent circuit has zero potential. Port 2





Dr. Vahid Nayyeri





When the Wilkinson power divider is driven at port 1 and the outputs are matched, no power is dissipated in the resistor. Thus the divider is lossless when the outputs are matched; only reflected power from ports 2 or 3 is dissipated in the resistor. Since $S_{23} = S_{32} = 0$, ports 2 and 3 are isolated.

Example 7.2 of Pozar.

Unequal Power Division and N-Way Wilkinson Dividers





An N-way, equal-split Wilkinson Power Divider

All ports are matched, with isolation between all ports.





Disadvantage: crossovers among the resistors, result in difficult fabrication process.

Solution: using stepped multiple sections.



Four Port Networks (Directional Couplers)

Pozar (page 320-322, 4rd Ed.) shows that a matched, reciprocal, lossless four-port network is possible, and that it has directional coupling between pairs of ports.

There are two possible forms of [S] for a directional coupler, one with outputs differing by 90° in phase and the other with outputs differing by 180° in phase.

Any 90° coupler can be made into a 180° coupler by adding a 90° transmission to one port, and *vice versa*.. The 90° coupler is referred to as a quadrature hybrid, and can be created using directly connected branch lines between two transmission lines or by means of coupled transmission lines.







Dr. Vahid Nayyeri

Symmetrical Coupler



Coupling, Directionality and Isolation

Coupling = $C = 10\log(P1/P3) = -20\log\beta dB$

Directivity = D = 10 log (P3/P4) = $20\log\beta/|S_{14}| dB$

Isolation = I = $10\log(P1/P4) = -20\log|S_{14}| dB$

Insertion loss= IL = $10\log(P1/P2) = -20\log|S_{12}| dB$

$$I = D + C \, \mathrm{dB}$$



Dr. Vahid Nayyeri

- A fraction of a wave traveling from port 1 to port 2 via the transmission line is coupled to port 3, but not to port 4.
- A fraction of a wave traveling from port 2 to port 1 is coupled to port 4, but not to port 3.
- The same coupling exists to transmission line 1-2 for waves traveling on line 4-3.



Symbols for directional couplers.

The use of a directional coupler is typically to sample the forward and/or reflected wave on a transmission line.

| Recalling the definition of <i>Coupling</i> , <i>Directivity</i> and | |
|--|---|
| Isolation factors. | C and IL can be measured directly, but the |
| Coupling = $C = 10\log(P_1/P_3)$ | power level at the port 4 may be small |
| Directivity = $D = 10 \log(P_3/P_4)$ | enough to make this difficult, particularly if the signal coupled from the |
| Isolation = $I = 10\log(P_1/P_4)$ | input to reverse output port 4 is masked by a reflected wave from an imperfectly |
| Insertion loss = $IL = 10\log(P1/P2)$ | matched load at port 2. |

Example: Consider a 20 dB coupler (C = 20 dB) with 30 dB directivity (D = 30 dB) connected to a load with a 15 dB return loss (RL = 15 dB).

The power at the reverse coupled port 4 resulting from the incident power at port 1 will be D+C=50 dB below the incident power, while the power at the same port resulting from the load reflection at port 2 will be RL+C=35 dB below the incident power.

Hence the reflected power adequately masks the power that defines the directivity D.

The Quadrature (90°) Hybrid Directional Couplers

- A 3 dB directional coupler with a 90° phase difference in the outputs of the through and coupled arms.
- Exist in the form of branch-line, coupled line and Lange (interdigitated). $z_0/\sqrt{2}$

Dr. Vahid Nayyeri

Decomposition of the coupler into even- and odd-mode excitations.

For the even-mode circuit,

We can then convert the ABCD matrix to S parameters, which are equivalent of the reflection and transmission coefficients. Thus,

$$\begin{split} \Gamma_e &= \frac{A+B-C-D}{A+B+C+D} = \frac{(-1+j-j+1)/\sqrt{2}}{(-1+j+j-1)/\sqrt{2}} = 0 \\ T_e &= \frac{2}{A+B+C+D} = \frac{2}{(-1+j+j-1)/\sqrt{2}} = \frac{-1}{\sqrt{2}}(1+j) \end{split}$$

For the odd-mode circuit,
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{o} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & j \\ j & 1 \end{bmatrix}$$

Then, $\Gamma_{o} = 0$ $T_{o} = \frac{1}{\sqrt{2}} (1-j)$
So,
 $B_{1} = 0$ (port 1 is matched)
 $B_{2} = -\frac{j}{\sqrt{2}}$ (half - power, -90° phase shift from port 1 to 2)
 $B_{3} = -\frac{1}{\sqrt{2}}$ (half - power, -180° phase shift from port 1 to 3)
 $B_{4} = 0$ (no power to port 4)
The [S] matrix is given by $[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$

Dr. Vahid Nayyeri

A practical microstrip quadrature hybrid prototype.

Some practical design issues:

1. Limited bandwidth: due to the nature of quarter-wave line. 10-20% BW Multisection design will help.

2. The effect of discontinuity at the junctions: shunt arms are usually lengthened by 10° - 20°.

Example 7.5 of Pozar

Frequency response

Coupled-Line Directional Couplers

Various geometries

Dr. Vahid Nayyeri

Even mode excitation: E-field symmetric about the center line

C₁₂ is opencircuited

 $C_e = C_{11} = C_{22}$, assuming the two strips are identical in size and location.

Odd mode excitation

 $Z_{0o} = \frac{1}{v_p C_o}$

• Z_{0e} (Z_{0o}) is the characteristic impedance of one of the strip conductors relative to ground when the coupled line is operated in the even (odd) mode.

• An *arbitrary* excitation of a coupled line can always be treated as a *superposition* of appropriate amplitudes of even and odd modes.

• For TEM lines, analytical techniques can be used to evaluate the capacitance per unit length of line, and the even- and odd-mode characteristic impedances can then be determined. For quasi-TEM lines, numerical or quasi-static techniques have to be used to find the results.

Design of Coupled-Line Couplers: using design graphs

Edge-coupled stripline

coupled microstrip lines

AMPLE 7.6 IMPEDANCE OF A SIMPLE COUPLED LINE

For the broadside coupled stripline geometry of Figure 7.26b, assume $W \gg S$ and $W \gg b$, so that fringing fields can be ignored, and determine the even- and odd-mode characteristic impedances.

Solution

We first find the equivalent network capacitances, C_{11} and C_{12} (because the line is symmetric, $C_{22} = C_{11}$). The capacitance per unit length of broadside parallel lines with width W and separation d is

$$\bar{C} = \frac{\epsilon W}{d} \, \mathrm{F/m},$$

where ϵ is the substrate permittivity. This formula ignores fringing fields.

 C_{11} is formed by the capacitance of one strip to the ground planes. Thus the capacitance per unit length is

$$\bar{C}_{11} = \frac{2\epsilon_r \epsilon_0 W}{b-s} \text{ F/m.}$$

The capacitance per unit length between the strips is

$$\bar{C}_{12} = \frac{\epsilon_r \epsilon_0 W}{S} \text{ F/m.}$$

Then from (7.68) and (7.70), the even- and odd-mode capacitances are

$$\bar{C}_e = \bar{C}_{11} = \frac{2\epsilon_r \epsilon_0 W}{b-S} \text{ F/m},$$
$$\bar{C}_o = \bar{C}_{11} + 2\bar{C}_{12} = 2\epsilon_r \epsilon_0 W \left(\frac{1}{b-S} + \frac{1}{S}\right) \text{ F/m}.$$

The phase velocity on the line is $v_p = 1/\sqrt{\epsilon_r \epsilon_0 \mu_0} = c/\sqrt{\epsilon_r}$, so the characteristic impedances are

$$Z_{0e} = \frac{1}{v_p \bar{C}_e} = \eta_0 \frac{b - S}{2W\sqrt{\epsilon_r}},$$

$$Z_{0o} = \frac{1}{v_p \bar{C}_o} = \eta_0 \frac{1}{2W\sqrt{\epsilon_r}[1/(b - S) + 1/S]}.$$

Design of Coupled Line Couplers

• One port driven with a 2V voltage generator (with internal impedance of Z_0) with other three ports terminated in Z_0 .

- A ground conductor is the common ground to both strip conductors.
- Design goals: port 1 is matched and port 4 is isolated.

Apply the even-odd mode analysis (avoiding the use of reflection and transmission coefficients).

Dr. Vahid Nayyeri

For symmetry, we have:

Even-mode

$$I_1^e = I_3^e$$
 $I_4^e = I_2^e$
 $V_1^e = V_3^e$ $V_4^e = V_2^e$

Odd-mode

$$I_1^o = -I_3^o \qquad I_4^o = -I_2^o$$
$$V_1^o = -V_3^o \qquad V_4^o = -V_2^o$$

The input impedance at port 1 is:

$$Z_{in} = \frac{V_1}{I_1} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o}$$

 Z_{0e} Z_0 +VThe even-mode circuits. Zo 11-0 $+V_{2}^{0}$ Z_{0o} Z_0 $+V_{1}^{0}$ $+V_{2}^{0}$

The odd-mode circuits.

Task: write the voltages and currents in terms of Z_{0e} and Z_{0o} .

Based on voltage division, we have

Meanwhile, the input impedance at port 1 for even and odd modes

are:

$$Z_{in}^{e} = Z_{0e} \frac{Z_{0} + jZ_{0e} \tan \theta}{Z_{0e} + jZ_{0} \tan \theta} \qquad Z_{in}^{o} = Z_{0o} \frac{Z_{0} + jZ_{0o} \tan \theta}{Z_{0o} + jZ_{0} \tan \theta}$$
If we let $Z_{0} = \sqrt{Z_{0e} Z_{0o}}$

The expression for Z_{in} is then given as,

$$Z_{in}^{e} = Z_{0e} \frac{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan\theta}{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan\theta} \qquad Z_{in}^{o} = Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0o}} \tan\theta}{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan\theta}$$

$$L_{in}^{o} = Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0e}} \tan\theta}{\sqrt{Z_{0o}} + j\sqrt{Z_{0e}} \tan\theta}$$

$$L_{in}^{o} = Z_{0o} \frac{\sqrt{Z_{0e}} + j\sqrt{Z_{0e}} \tan\theta}{\sqrt{Z_{0e}} + j\sqrt{Z_{0e}} \tan\theta}$$

Now, let us look at the coupling between the two lines, shown at port 3.

$$V_{3} = V_{3}^{e} + V_{3}^{o} = V_{1}^{e} - V_{1}^{o} = V \left[\frac{Z_{in}^{e}}{Z_{in}^{e} + Z_{0}} - \frac{Z_{in}^{o}}{Z_{in}^{o} + Z_{0}} \right]$$

Plug in the expression of Z_{in}^e and Z_{in}^o

$$V_{3} = V \frac{j(Z_{0e} - Z_{0o})\tan\theta}{2Z_{0} + j(Z_{0e} + Z_{0o})\tan\theta}$$

Now, we can define *C* as

$$C = \frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}}$$

Dr. Vahid Nayyeri

Then, $\sqrt{1-C^2} = \frac{2Z_0}{Z_{00} + Z_{00}}$ So there is coupling between the lines that is periodic in the line electrical length. The 1 coupled line network is generally designed for a line length of $\lambda/4$, the first maximum of coupling. For these conditions the analysis yields, for a voltage coupling ratio C, the required impedances

So that,
$$V_3 = V \frac{jC \tan \theta}{\sqrt{1 - C^2} + j \tan \theta}$$

$$\int_{0}^{1} \frac{|V_2|^2}{|V|^2} \frac{|V_3|^2}{|V|^2}$$

$$\int_{0}^{1} \frac{\pi}{2} \frac{\pi}{2} \frac{3\pi}{2} 2\pi \frac{|V_3|^2}{|V|^2}$$

Coupled and through port voltages (squared) versus frequency for the coupled-line coupler.

$$Z_{0e} = Z_0 \sqrt{\frac{1+C}{1-C}}$$
 $Z_{0o} = Z_0 \sqrt{\frac{1-C}{1+C}}$

We can show that,
$$V_4 = V_4^e + V_4^o = V_2^e - V_2^o = 0$$

and $V_2 = V_2^e + V_2^o = V \frac{\sqrt{1 - C^2}}{\sqrt{1 - C^2}} \cos \theta + j \sin \theta$

Example 7.7 of Pozar.

Design notes:

For microstrip, these can be read off a nomogram, simplifying the design of practical couplers. Note that the assumption of equal propagation velocities for the even and odd modes is not accurate for microstrip, so microstrip couplers are generally not as directive as couplers built with TEM transmission lines such as coaxial cable and stripline.

In general, line spacings required for 3 and 6 dB couplers are too close to maintain good tolerances with single edge-coupled transmission lines. Also, the bandwidth limitations of quarter-wave couplers are not suited for practical broadband circuits.

Dr. Vahid Nayyeri

Multisection Coupled Line Couplers

Very Important Self Study: Pozar, Chapter 7, Section 6

Coupling versus frequency for the three-section binomial coupler

The Lange Couplers

- Coupled-line couplers are not suitable to achieve coupling factors of 3 dB or 6 dB, due to the loose coupling.
- Tight coupling can be achieved by the special layout of the coupled lines, so that the fringing fields at the edge of the lines can contribute to the coupling.

The interdigitated Lange coupler

The unfolded Lange coupler

Dr. Vahid Nayyeri

Fabricated Lange Coupler

The Lange couplers has the following features:

- There is a 90° phase difference between the output lines (ports 2 and 3)
- Difficult to fabricate the bonding wires due to the narrow spacing between the lines.

For the sake of simplicity, the unfolded Lange coupler is analyzed.

Equivalent circuits for the unfolded Lange Coupler.

Four-wire coupled line model.

Approximate two-wire coupled line model.

Assumption is made that each line couples only to its nearest neighbor.

We are to determine Ze4 and Zo4 in terms of Ze and Zo

Dr. Vahid Nayyeri

Solve for C_{e4} and C_{o4} with C_e and C_o , we have

$$Z_{e4} = \frac{Z_{0o} + Z_{0e}}{3Z_{0o} + Z_{0e}} Z_{0e} \qquad Z_{o4} = \frac{Z_{0o} + Z_{0e}}{3Z_{0e} + Z_{0o}} Z_{0o}$$

Just like the coupled-line couplers, we have

$$Z_0 = \sqrt{Z_{e4} Z_{o4}} = \sqrt{\frac{Z_{0e} Z_{0e} (Z_{0e} + Z_{0e})^2}{(3Z_{0e} + Z_{0e})(3Z_{0e} + Z_{0e})}}$$

$$C = \frac{Z_{e4} - Z_{o4}}{Z_{e4} + Z_{o4}}$$

C is the coupling coefficient.

Dr. Vahid Nayyeri

For design purpose, we can obtain

$$Z_{0e} = \frac{4C - 3 + \sqrt{9 - 8C^2}}{2C\sqrt{(1 - C)/(1 + C)}} Z_0$$

$$Z_{0o} = \frac{4C + 3 - \sqrt{9 - 8C^2}}{2C\sqrt{(1 + C)/(1 - C)}} Z_0$$

The 180° Hybrid

- The two outputs are either in phase or with a **180**° phase difference.
- A signal applied to port 1 is evenly divided into two in-phase components at port 2 and 3, with port 4 isolated.
- A signal applied to port 4 is equally split into two out-of-phase components at port 2 and 3, with port 1 isolated.

• When operated as a combiner, with inputs at ports 2 and 3, the sum of the inputs will be formed at port 1 (the sum port), while the difference will be formed at port 4 (the difference port).

Ring Hybrid (rat-race): a typical 180° Hybrid

Similar to branch-line coupler. Can be easily constructed in planar (microstrip or stripline) form.

Dr. Vahid Nayyeri

Even-Odd Mode Analysis of the Ring Hybrid

Dr. Vahid Nayyeri

$$B_1 = \frac{1}{2}\Gamma_e + \frac{1}{2}\Gamma_o \qquad B_2 = \frac{1}{2}T_e + \frac{1}{2}T_o \qquad B_3 = \frac{1}{2}\Gamma_e - \frac{1}{2}\Gamma_o \qquad B_4 = \frac{1}{2}T_e - \frac{1}{2}T_o$$

ABCD matrix for the even- and odd-mode circuits are

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_{e} = \begin{bmatrix} 1 & j\sqrt{2} \\ j\sqrt{2} & -1 \end{bmatrix} \qquad \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{o} = \begin{bmatrix} -1 & j\sqrt{2} \\ j\sqrt{2} & 1 \end{bmatrix}$$

Which lead to,

and,

$$B_1 = 0$$
 $B_2 = \frac{-j}{\sqrt{2}}$ $B_3 = \frac{-j}{\sqrt{2}}$ $B_4 = 0$

Dr. Vahid Nayyeri

Dr. Vahid Nayyeri

Following the same ABCD-based analysis

$$B_1 = 0$$
 $B_2 = \frac{J}{\sqrt{2}}$ $B_3 = \frac{-J}{\sqrt{2}}$ $B_4 = 0$

Other Types of Hybrid

A tapered coupled line hybrid

